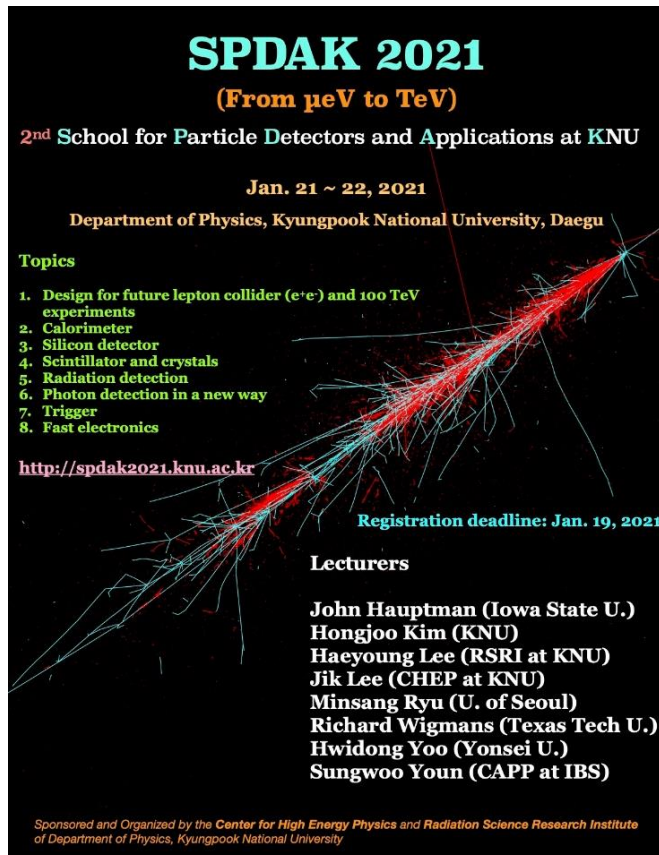


# Introduction of Fast Electronics

**RYU, Min Sang**  
**University of Seoul**



**SPDAK 2021**  
**(From  $\mu\text{eV}$  to TeV)**  
2<sup>nd</sup> School for Particle Detectors and Applications at KNU  
Jan. 21 ~ 22, 2021  
Department of Physics, Kyungpook National University, Daegu

**Topics**

1. Design for future lepton collider ( $e^+e^-$ ) and 100 TeV experiments
2. Calorimeter
3. Silicon detector
4. Scintillator and crystals
5. Radiation detection
6. Photon detection in a new way
7. Trigger
8. Fast electronics

<http://spdak2021.knu.ac.kr>

Registration deadline: Jan. 19, 2021

**Lecturers**

John Hauptman (Iowa State U.)  
Hongjoo Kim (KNU)  
Haeyoung Lee (RSRI at KNU)  
Jik Lee (CHEP at KNU)  
Minsang Ryu (U. of Seoul)  
Richard Wigmans (Texas Tech U.)  
Hwidong Yoo (Yonsei U.)  
Sungwoo Youn (CAPP at IBS)


Sponsored and Organized by the Center for High Energy Physics and Radiation Science Research Institute of Department of Physics, Kyungpook National University

- ◆ Role of DAQ in HEP experiment
- ◆ Readout scheme for DAQ
- ◆ Fast electronics
  - Signal and Device impedance
  - Preamplifier
  - Fan-In and Fan-Out
  - Discriminator (LED & CFD)
  - Logic Unit for coincidence
  - TDC & ADC
- ◆ Summary


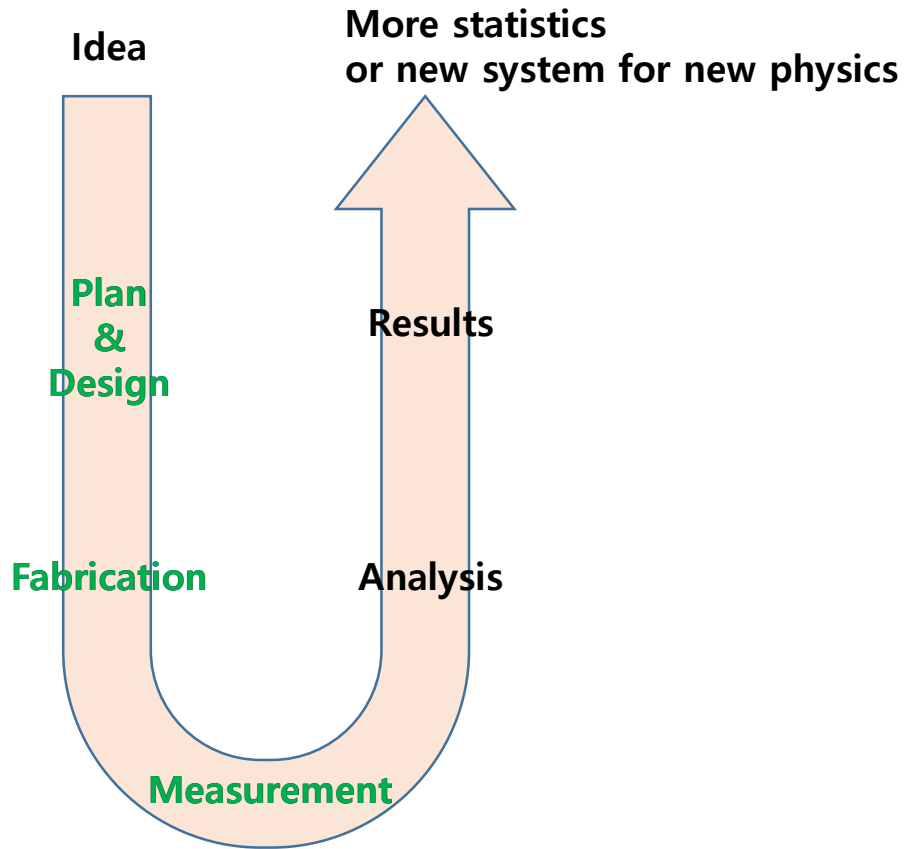
# Role of DAQ System in HEP experiment

How do we watch an event in HEP experiments?




Five Ws & Hows	Measurement of particle detection
Why	Why needs information about particles → to find out why they are existed and created
Plan & Design → Fabrication → Measurement	
How	How particle interacts with materials
Where	Position where interaction happens
When	Time when interaction happens
Who/Which	Which particles → PID
What	What characteristics of particles

We design, fabricate, test, and use the **readout system (or fast electronics)** for data acquisition (DAQ).


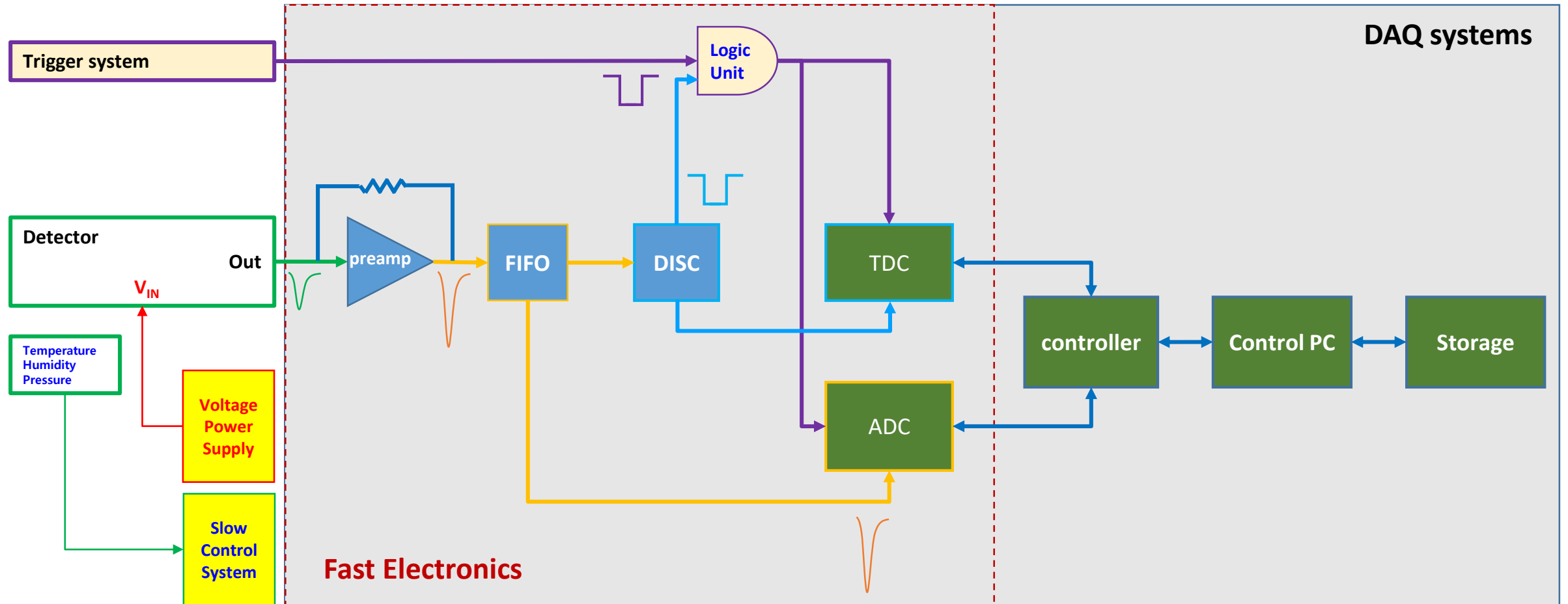
# Readout scheme for data acquisition (DAQ)



# Components of waveform

Base line  
Pulse height  
Pulse width


Proximal line: 10% of pulse height  
Mesial line: 50% of pulse height  
Distal line: 90% of pulse height

Rise time (or attack time) at leading edge  
Fall time (or decay time) at trailing edge  
→ These depend on the polarity of waveform.



Overshoot  
Undershoot  
Ringing

Time period

 [https://link.springer.com/chapter/10.1007/978-3-319-25448-7\\_7](https://link.springer.com/chapter/10.1007/978-3-319-25448-7_7)



# Charge of raw signal

  

Electric charge of analog signal with assumption:


$$Q(C) = \frac{V(V) \cdot t(s)}{2 \cdot R(\Omega)} = \frac{-0.1 V \cdot 20 ns}{2 \cdot 50 \Omega} = -20 pC$$




# Device impedances

A basic concept in the processing of pulses from radiation detectors is the impedance of the devices that comprise the signal-processing chain.

Input configuration

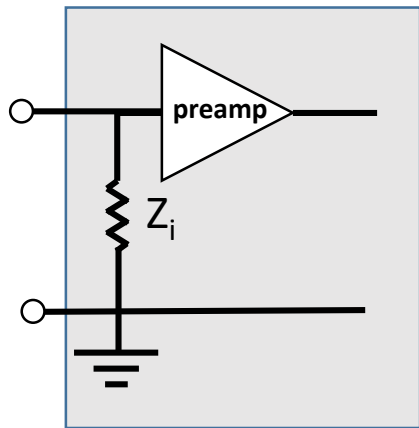

output configuration

 

Voltage ( $V_L$ ) appearing across a loading ( $Z_L$ ) by voltage-divider relation

$$V_L = V_S \frac{Z_L}{Z_0 + Z_L}$$

For the open-circuit or unloaded ( $Z_L = \infty$ ), voltage is  $V_L = V_S$ . → not for the real experiment

To preserve maximum signal level, one normally wants  $V_L$  to be as large a fraction of  $V_S$  as possible. For  $Z_L \gg Z_0$  then  $V_L \cong V_S$  → Fan-In & Fan-Out, Discriminator, ADC, etc

For  $Z_L = Z_0$  then  $V_L = V_S/2$  → Divider or Splitter



# Preamplifier

Role	converting a raw signal from the detector into output signal with gain
Location	placing close to the detector to reduce the noise and avoid the signal loss

## ✓ Specification for design


- Dynamic range
- Size of input signal
- Pulse pileup
- Signal-to-noise ratio
- Power consumption

## ✓ Configuration


- Voltage-sensitive preamplifiers
- Current-sensitive preamplifiers
- Charge-sensitive preamplifiers



# Voltage-sensitive preamplifiers

 

Design principle of V-sensitive preamp

 

Simplified realistic V-sensitive preamp

Signal voltage  $V_S$   
Voltage at the input stage of the amplifier  $V_a$   
Output voltage  $V_{out}$

$$V_a = V_S \frac{R_a}{R_S + R_a}$$

Any current drawn would decrease the potential drop across  $R_S$ . Ideally, its input resistance have to be infinite. But it can only be achieved up to a good approximation.

For  $R_a \gg R_S$  then  $V_a \cong V_S$   
then  $V_{out} = Gain \times V_a \approx Gain \times V_S$

Signal voltage  $V_S = Q/C_d$

$Q$ : collected charge on the readout electrode ( $Q = \int_0^{t_0} i_s(t) dt$ )

$C_d$ : combined detector and stray capacitance


$$\text{then } V_{out} \approx Gain \times \frac{Q}{C_d} = \frac{Gain}{C_d} \int_0^{t_0} i_s(t) dt$$

Since we are integrating the current to convert it into voltage,  **$C_d$  should discharge slower than the charge collection time  $t_d < R_a C_d$ .**






# Charge-sensitive preamplifiers

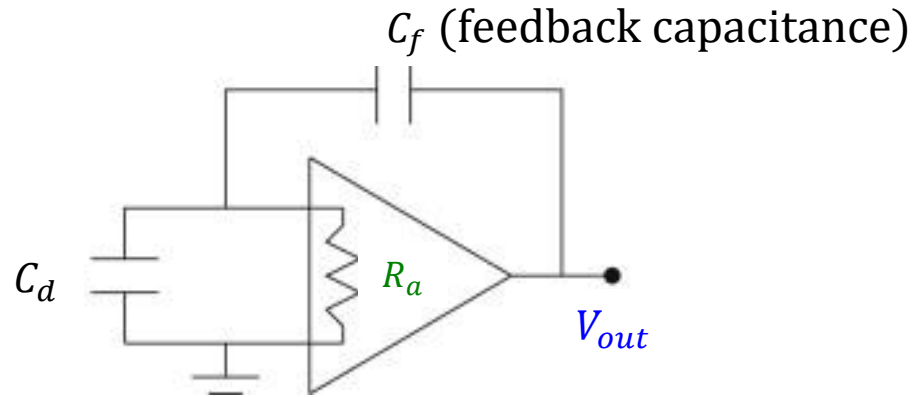

Basic principle of Q-sensitive preamp

 The dependence of a voltage-sensitive preamplifier on the input capacitance is a serious problem for many detection systems.  
 → to develop Q-sensitive preamplifiers




Simple Q-sensitive preamp

The charge ( $Q_d$ ) accumulated on the electrode ( $C_d$ ) is integrated on another capacitor ( $C_f$ ). Then the potential ( $V_f$ ) on that capacitor is then directly proportional to the original charge ( $Q_d$ ) on the detector.

$$V_{out} \propto \frac{Q_f}{C_f} \propto \frac{Q_d}{C_f}$$

 The condition that  $Q_f \approx Q_d$  can only be achieved if no current flows into the preamplifier's input with  $R_a \rightarrow \infty$ .





## CAEN N412 8ch Fast Amplifier

### INPUTS:

- 50 $\Omega$  impedance.
- Reflection coefficient:  $\leq 6\%$  over input dynamic range.

- Quiescent voltage:  $< \pm 5$  mV.

### OUTPUTS:

- Risettime:  $\leq 3.0$  ns.
- Falltime:  $\leq 2.0$  ns.
- Maximum positive amplitude (linear): 400 mV (50 $\Omega$  impedance).
- Maximum negative amplitude (linear): -4 V (50 $\Omega$  impedance).
- Overshoot:  $\pm 10\%$  for input risetimes of 2 ns and with the 2nd output terminated in 50 $\Omega$ .
- Quiescent voltage adjustable (via front panel trimmer for each channel) in the range from -20 mV to +50 mV.


### GENERAL:

- Gain: fixed 10  $\pm$  3%, non-inverting.
- Coupling: direct.
- I/O delay:  $\leq 12$  ns.
- Noise: less than 1 mV, referred to input.
- Interchannel crosstalk: better than -56 dB in the worst test condition, and with both the outputs of the tested channel terminated in 50 $\Omega$ .
- Bandwidth:
  - 160 MHz (with both the channel's outputs terminated in 50 $\Omega$ );
  - 180 MHz (single ended output).



 
# Fan-In and Fan-Out (FIFO)


**Fan-in:** maximum number of input signals feeding into the input of a logic system



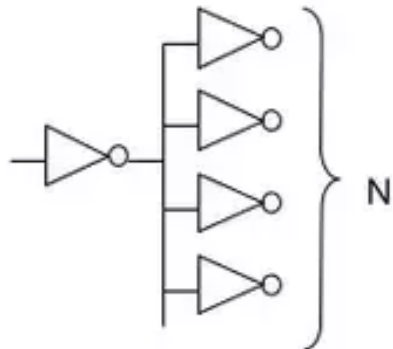
**Fan-out:** maximum number of output signals from the output of a logic system



# Fan-In and Fan-Out (FIFO)

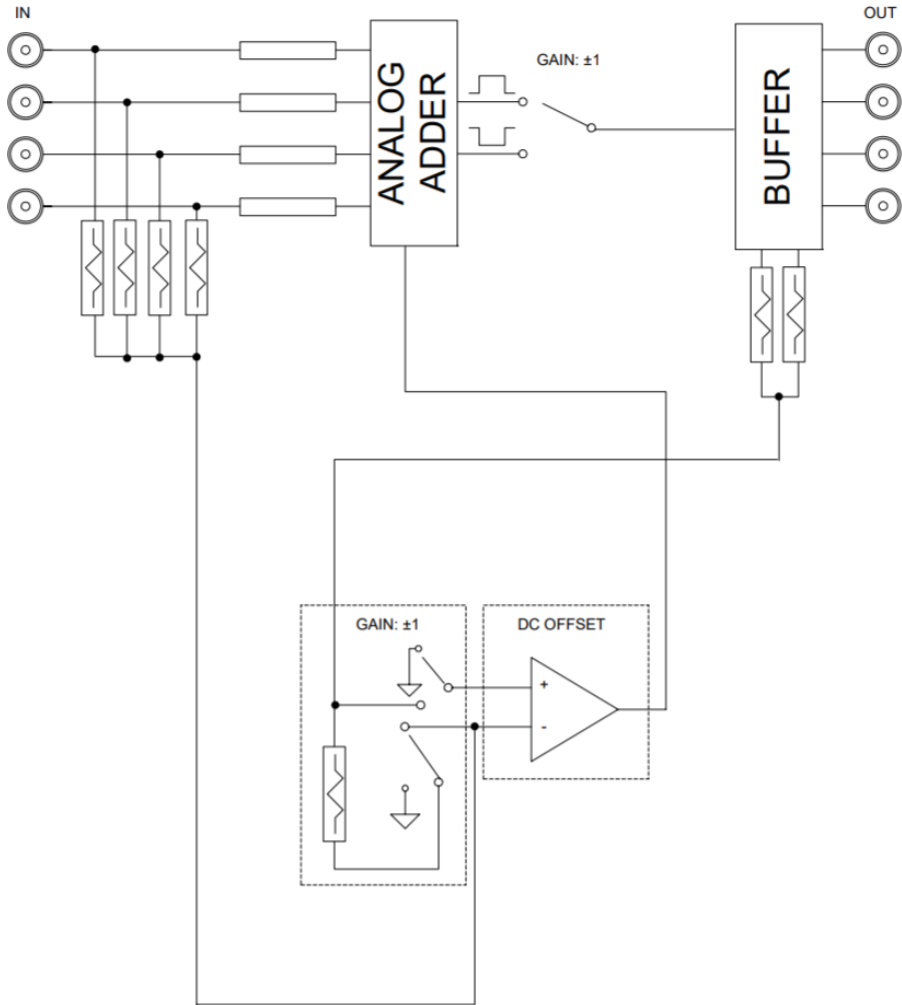


CAEN N625 Quad Linear Fan In / Fan Out

 
 
# Discriminator (DISC)


**Role:** generating the logical output pulse when the input pulse exceeds the discriminator preset level

→ If input voltages **exceeds the threshold value  $+V$**  then diode  $D_1$  conducts and **DISC generates the logical output pulses.**



# Timing jitter and walk

Timing jitter in a pulse

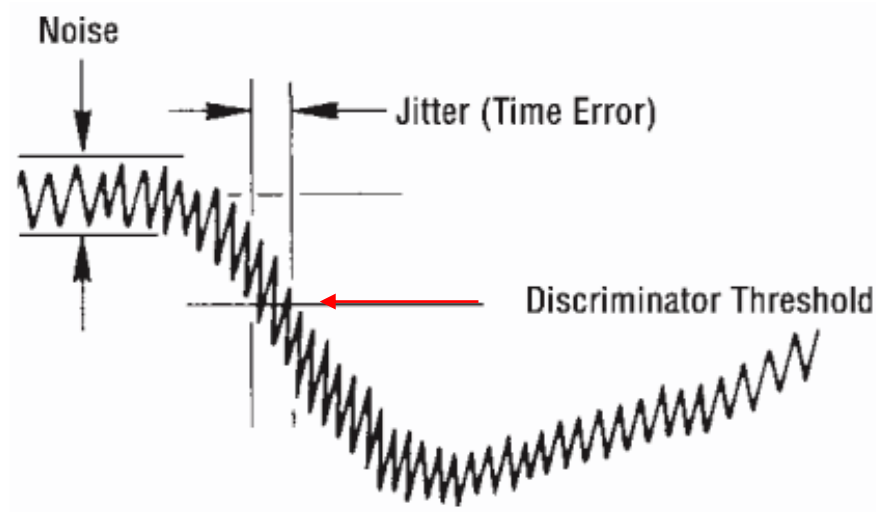


## The contribution of noise to the (Timing) Jitter

$$\text{Timing Jitter} = e_{\text{noise}} / (dV/dt)$$

$e_{\text{noise}}$ : voltage amplitude of the noise superimposed on the analog pulse

$dV/dt$ : slope of the signal when its leading edge crosses the discriminator threshold




Timing walk among pulses

 

“(Timing) Walk” is the **systematic dependence** of the time marker on the **amplitude of the input pulse**.



# LED and CFD

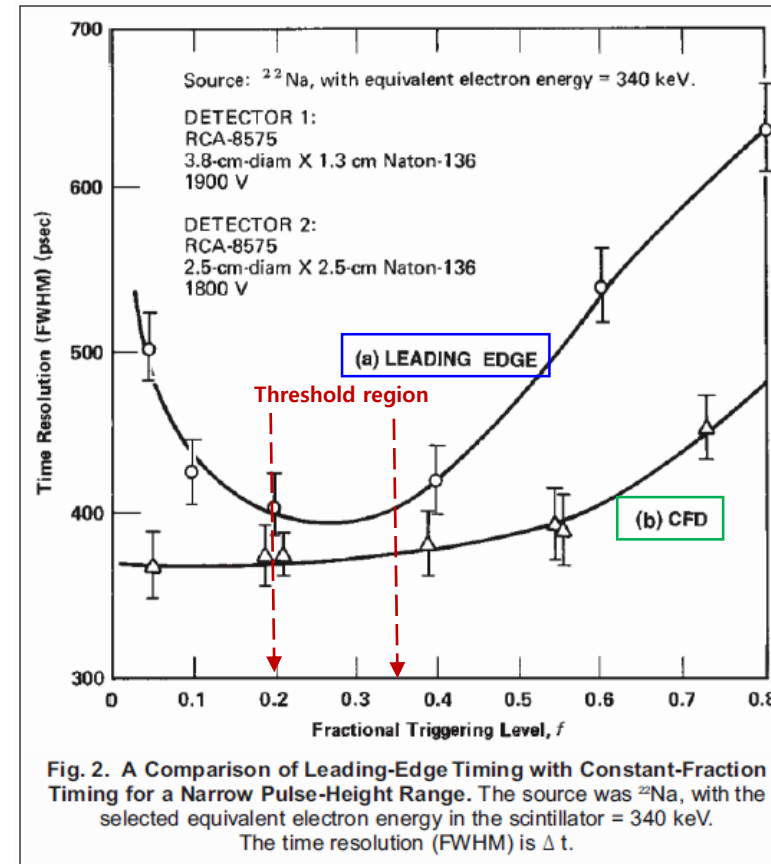 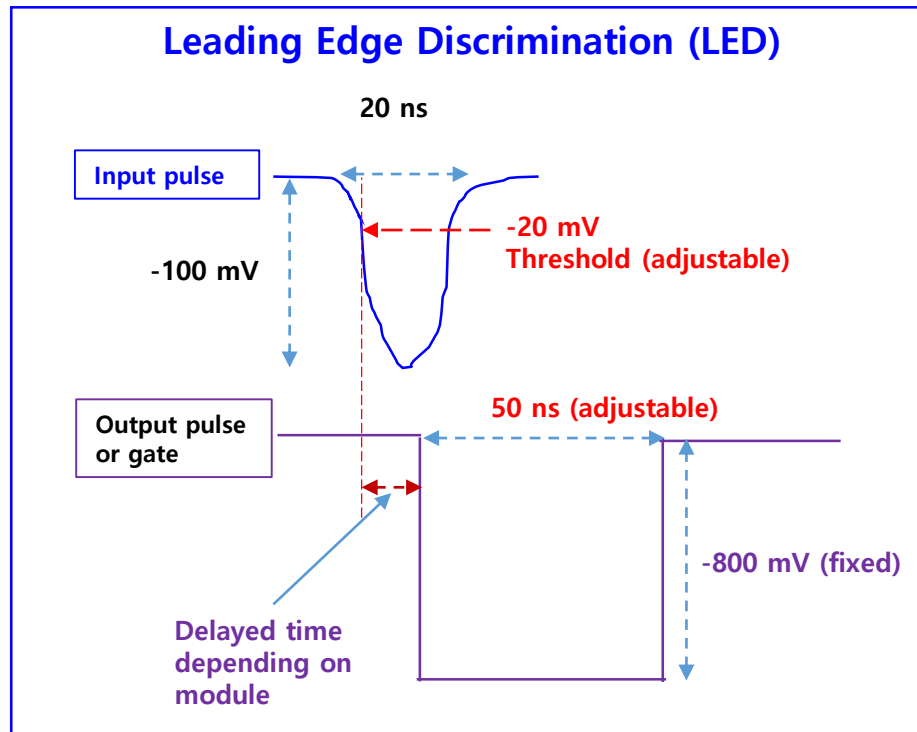

[http://www.peo-radiation-technology.com/wp-content/uploads/2015/09/ort\\_15\\_fast-timing-discriminators\\_datasheet\\_peo.pdf](http://www.peo-radiation-technology.com/wp-content/uploads/2015/09/ort_15_fast-timing-discriminators_datasheet_peo.pdf)


**Time resolution:  $\sigma_{\text{CFD}} < \sigma_{\text{LED}}$**


 
# Role of Logic Unit


**Role:** generating the gating pulse when the preset of logical algorithm against with inputs is true

**AND logic:**  $A \cdot B$  or  $A \wedge B$



INPUT		OUTPUT
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

**OR logic:**  $A + B$  or  $A \vee B$


 


INPUT		OUTPUT
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1





# Logic Unit

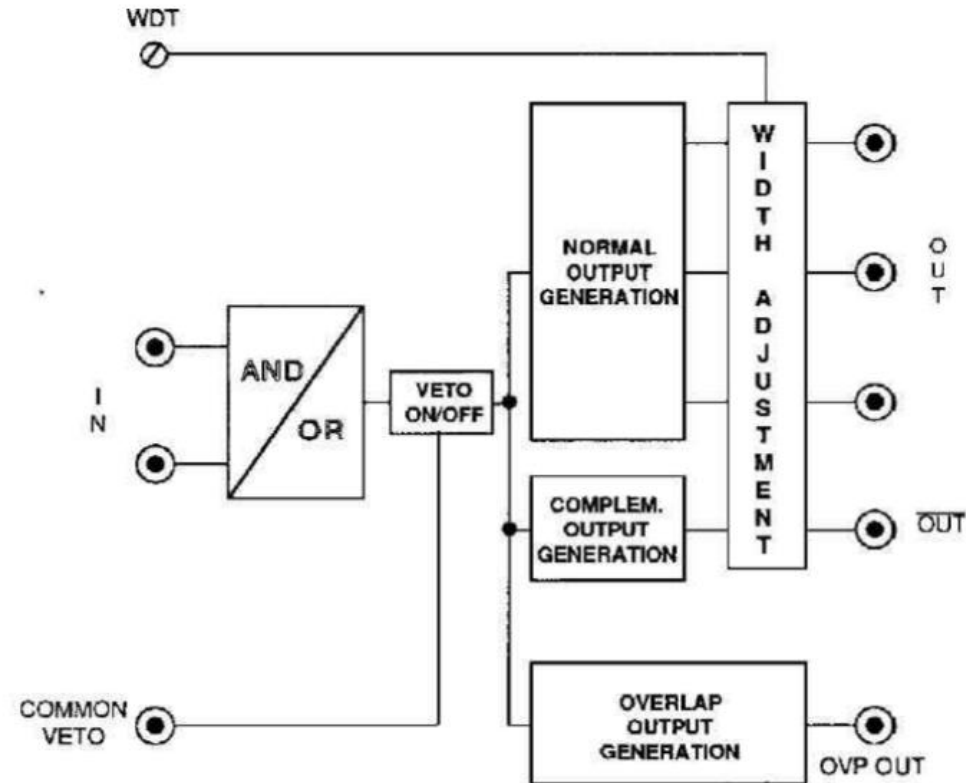 


**IMPORTANT NOTE:**  
Unused Outputs require a 50  $\Omega$  termination

CAEN N455 Quad Coincidence Logic Unit



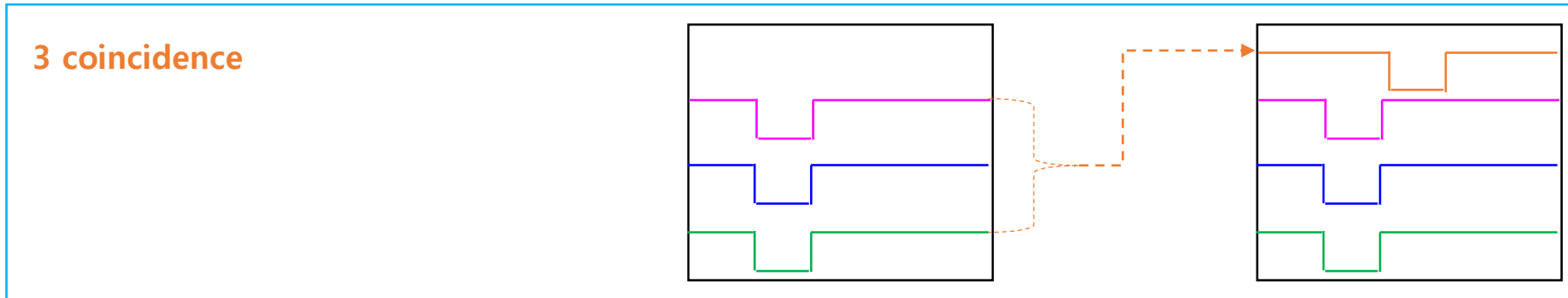
# Coincidence with 3 inputs

When events occur, the input signals from many detectors can be matched with Logic Unit.




## Coincidence with timing walk


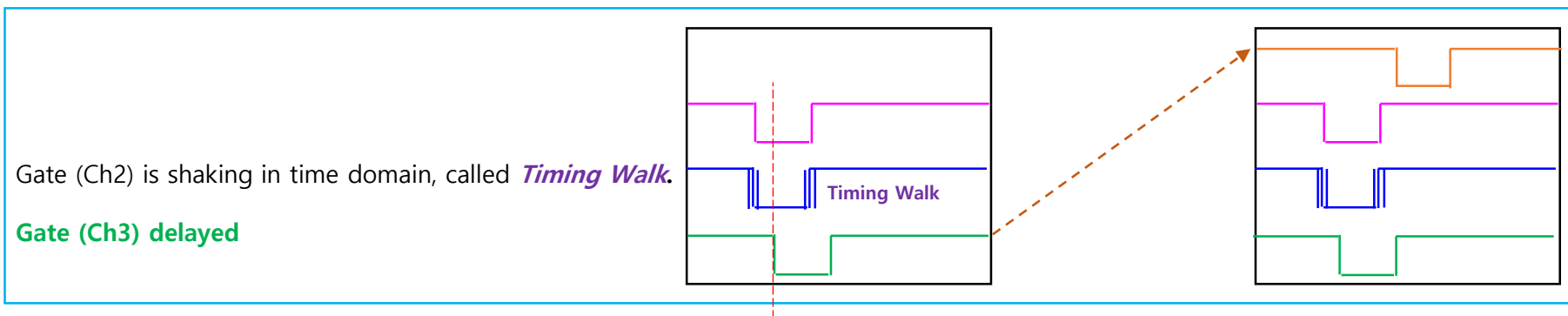

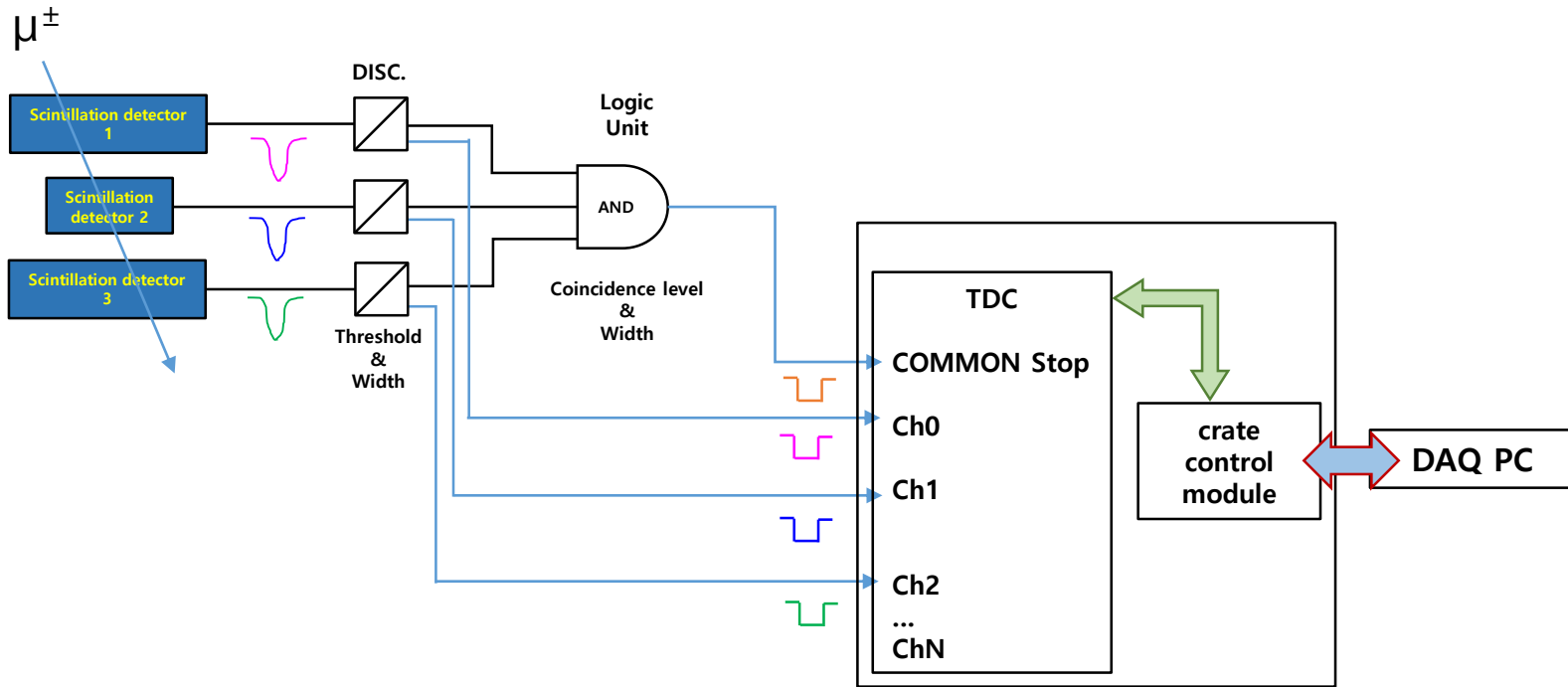
# Time measurements with TDC

Scintillation counter/detector:  
Scintillator + PhotoMultiplier Tube (PMT)



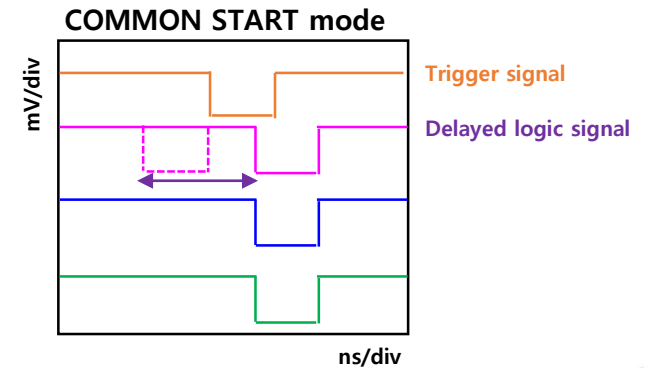 
Operation mode of TDC: COMMON STOP/START?



Time-to-Digital Converter (TDC)



# How to record time in TDC?

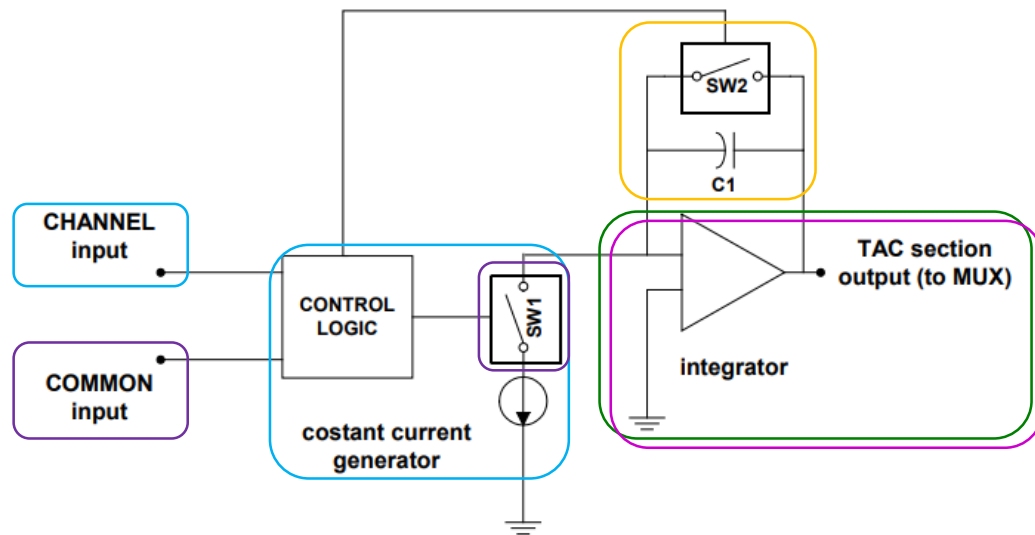

Block diagram of TAC section in CAEN V775N 16ch MultiEvent TDCs

A Start signal closes the **switch SW1** thus allowing a **constant current** to flow through an **integrator**; a Stop signal opens the **switch SW1** again.



The constant current generates a **linear ramp voltage** which is stopped at an **amplitude proportional to the time interval** between Start and Stop pulses.





After digitization the **SW2 switch** is closed by the CLEAR signal which allows the discharge of the **capacitor C1**.

Both the COMMON and CLEAR signals are controlled by the CONTROL LOGIC section.




# TDC and signal conversion timing

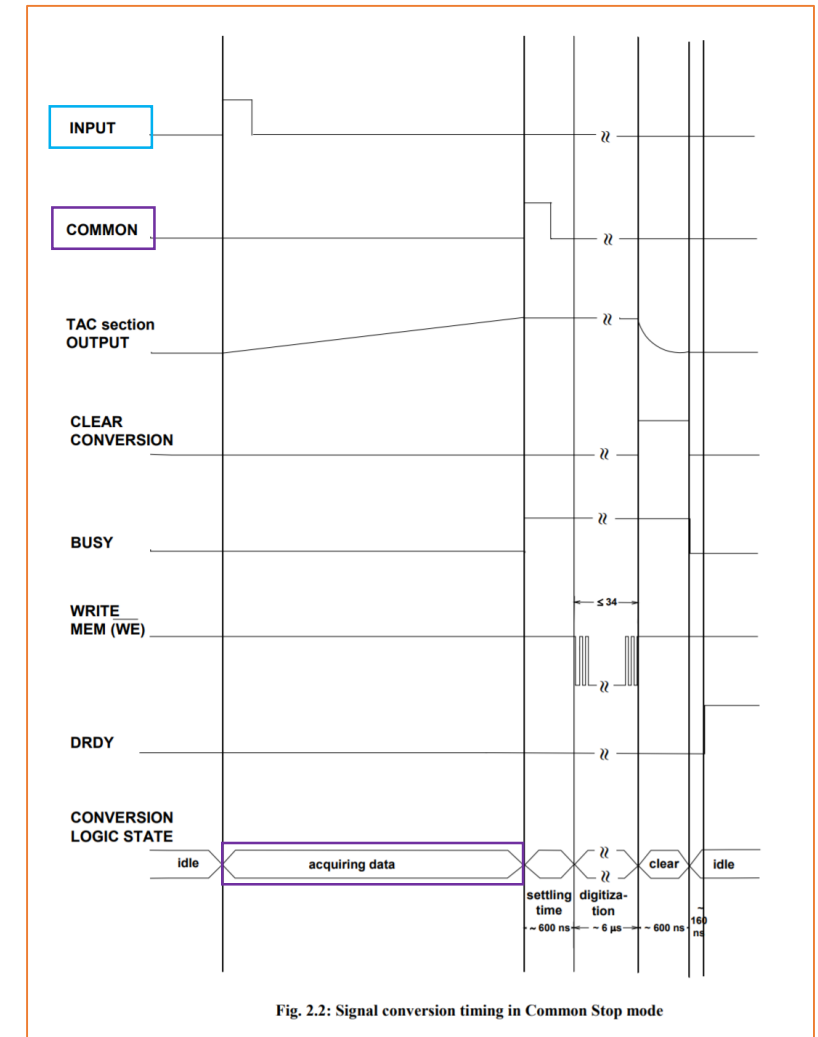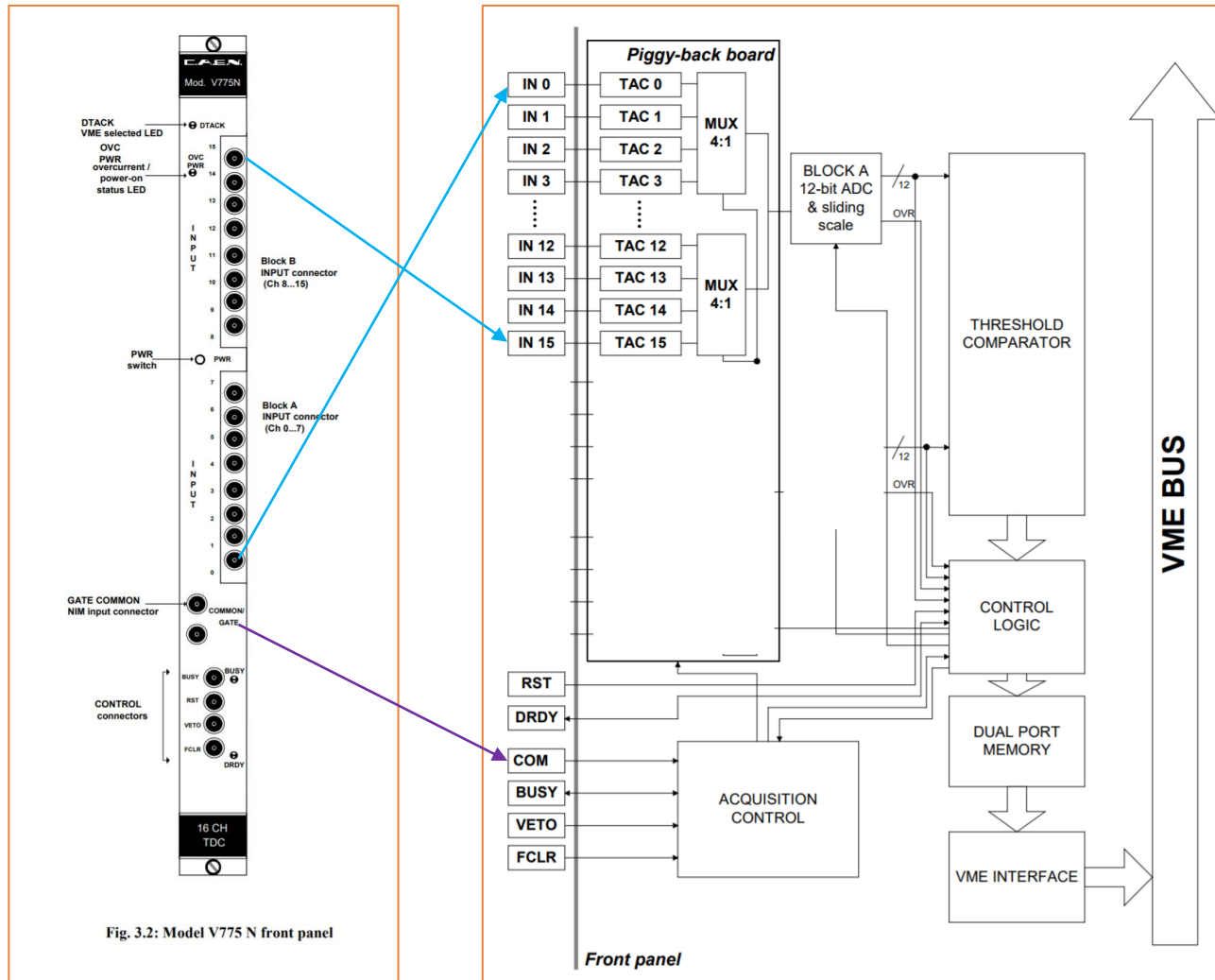

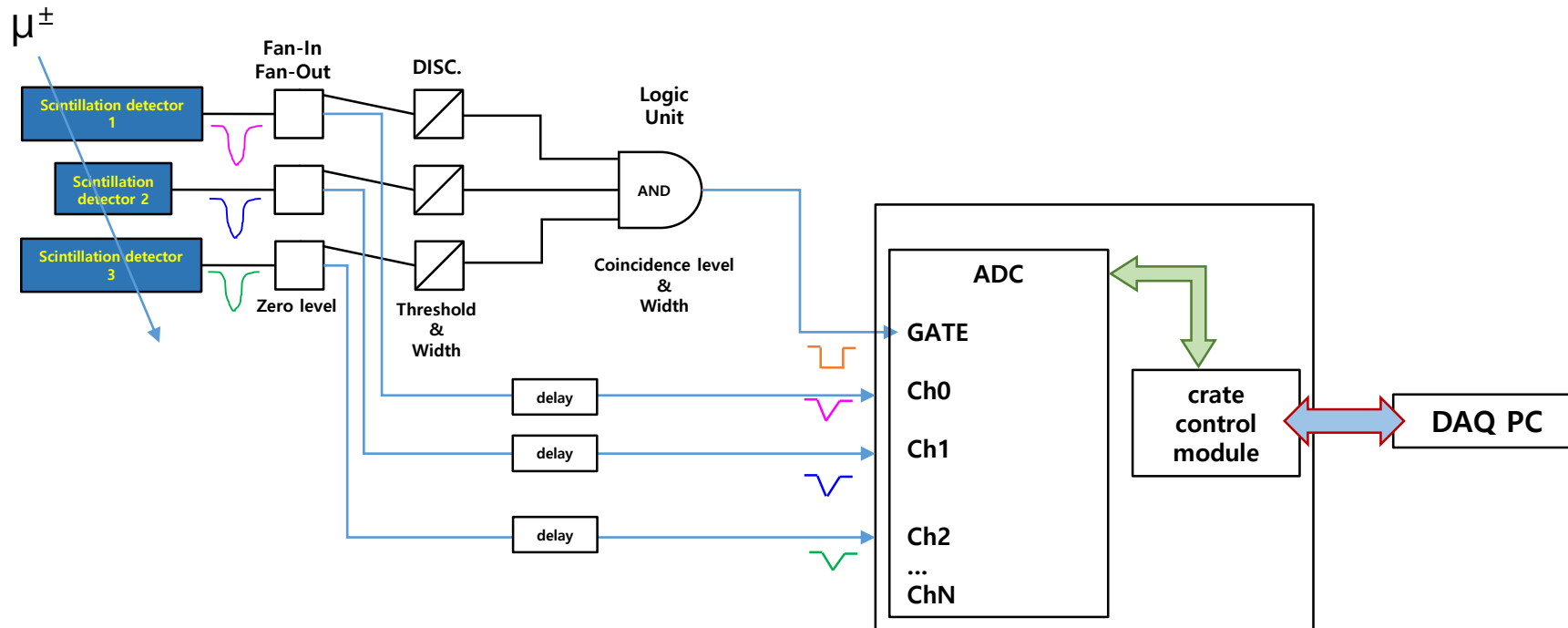
# Charge measurements with ADC


Scintillation counter/detector:  
Scintillator + PhotoMultiplier Tube (PMT)



Time domain of signals for ADC

 

# How to record charge in ADC?

 

## COMMON STOP mode

The **GATE signal** closes the **switch SW1** thus allowing the **capacitor C1** to be charged as the **diode D1** is forward-biased by the signal.



As the **SW1** is open again, the signal is digitized by the 12-bit ADCs.



After digitization the **SW2 switch** is closed by the CLEAR signal which allows the discharge of the **capacitor C1**.

Both the GATE and CLEAR signals are controlled by the CONTROL LOGIC section.

Block diagram of PEAK section in CAEN V1785 8ch Dual Range Peak ADC



# ADC and signal conversion timing

 


Fig. 3.1: Model V1785 front panel

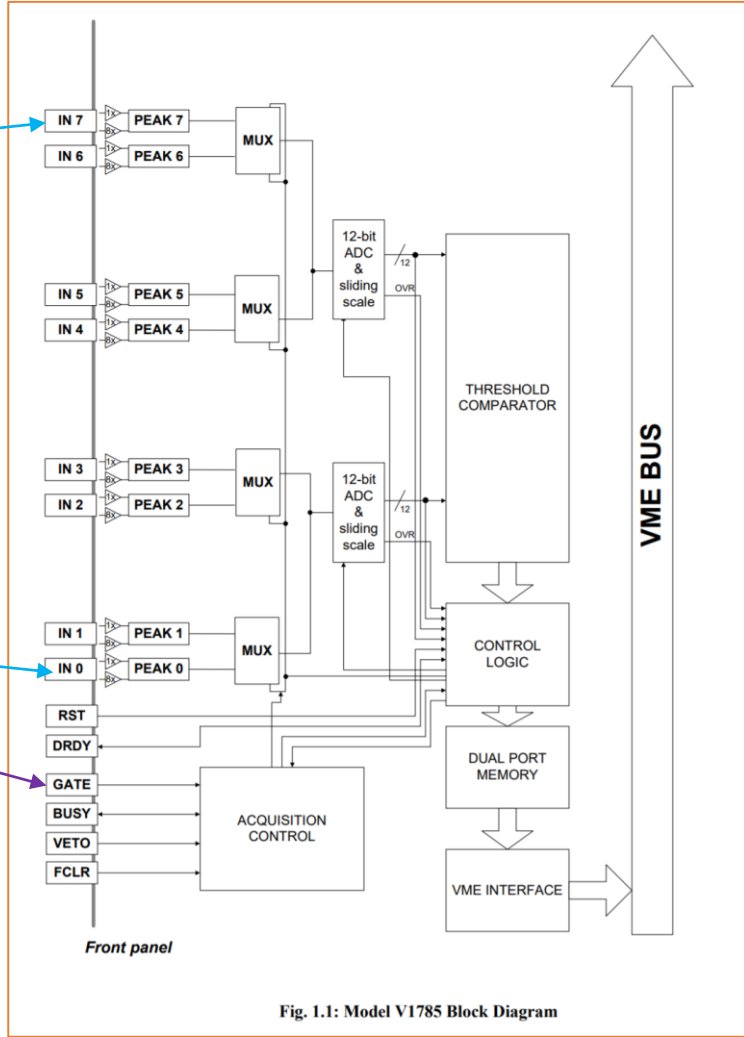


Fig. 1.1: Model V1785 Block Diagram

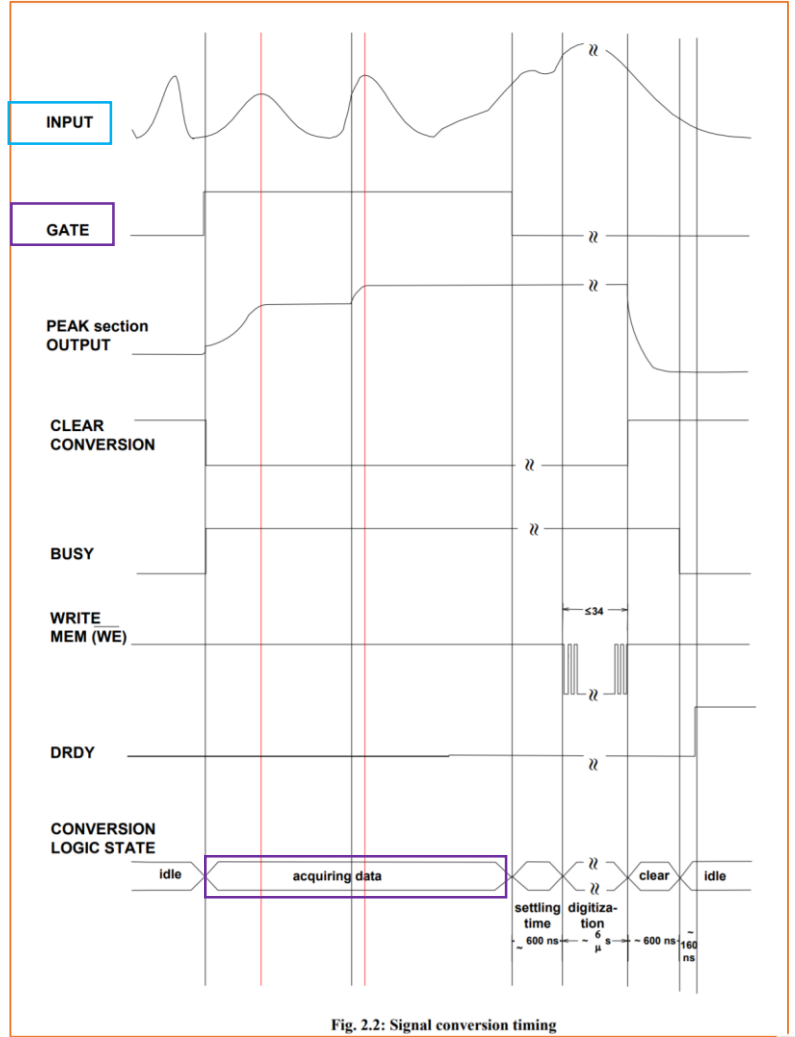


Fig. 2.2: Signal conversion timing

## CAEN V1785 8ch Dual Range Peak ADC

Dual input range: 0 ÷ 4 V / 0 ÷ 500 mV  
Gain: 1 mV/count and 125 uV/count for High and Low ranges




# Summary: Event in HEP experiment


“Fast Electronics” are a main component of particle detection system to see what happens in the HEP experiments.

First Pb collision of ALICE experiment at  $\sqrt{s} = 5.02$  TeV in 2018

<https://cds.cern.ch/record/2646381>

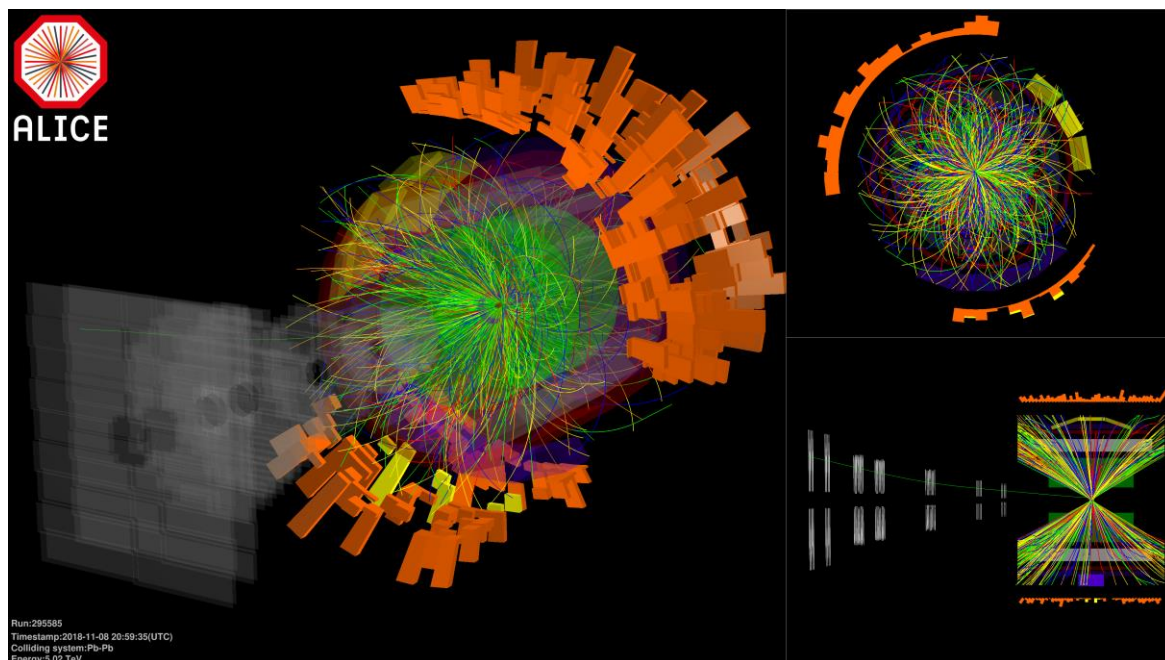


## RD51 Scalable Readout System (SRS)

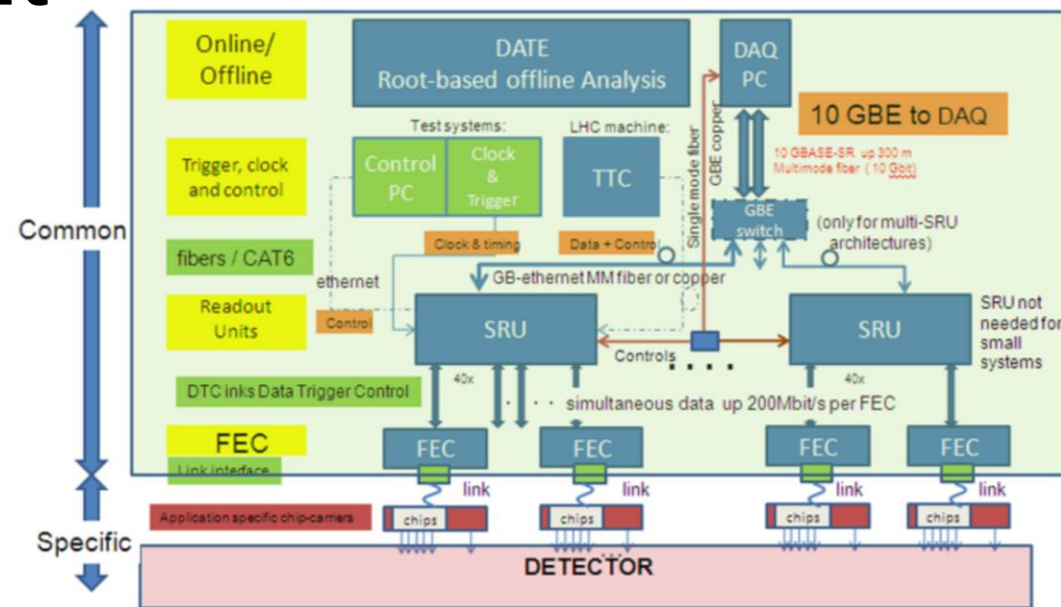

<https://indico.cern.ch/event/77597/contributions/2088463/attachments/1056845/1506857/RD51-SRS-Description.pdf>

## physical overview SRS of RD51

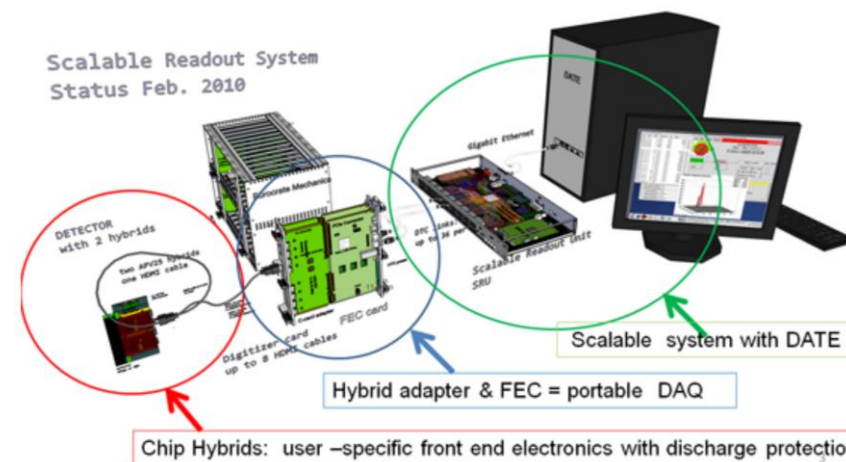

# Thank you